



DRAWING

ROOT

LAST\_MODIFIED=Mon Dec 2 10:55:03 1996


# CRATE LEVEL TRIGGER CARD

ROOT

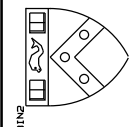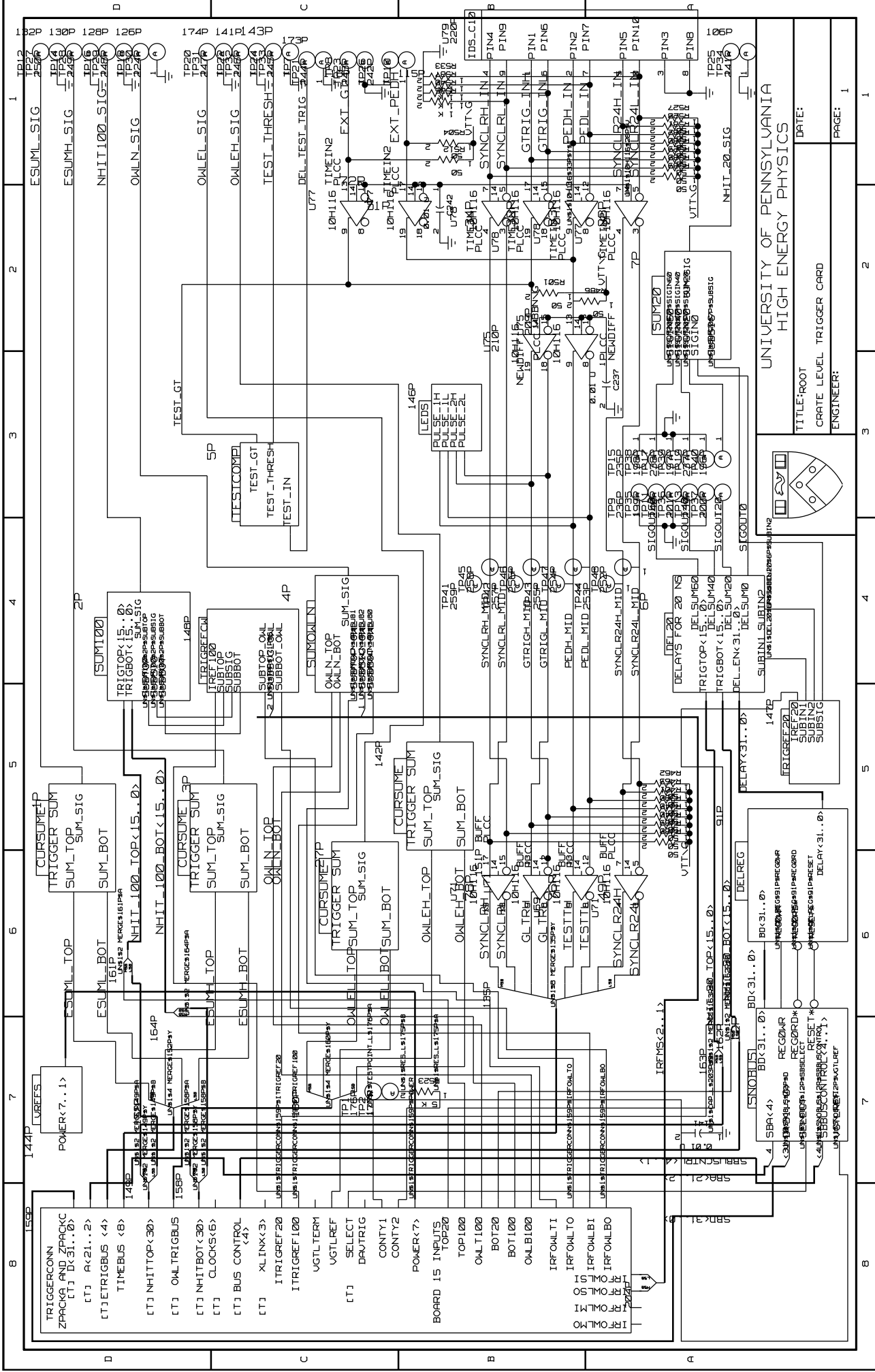


UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS

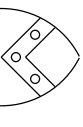
TITLE: ROOT  
CRATE LEVEL TRIGGER CARD  
ENGINEER: 1



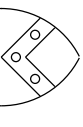
UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS



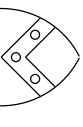
UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS



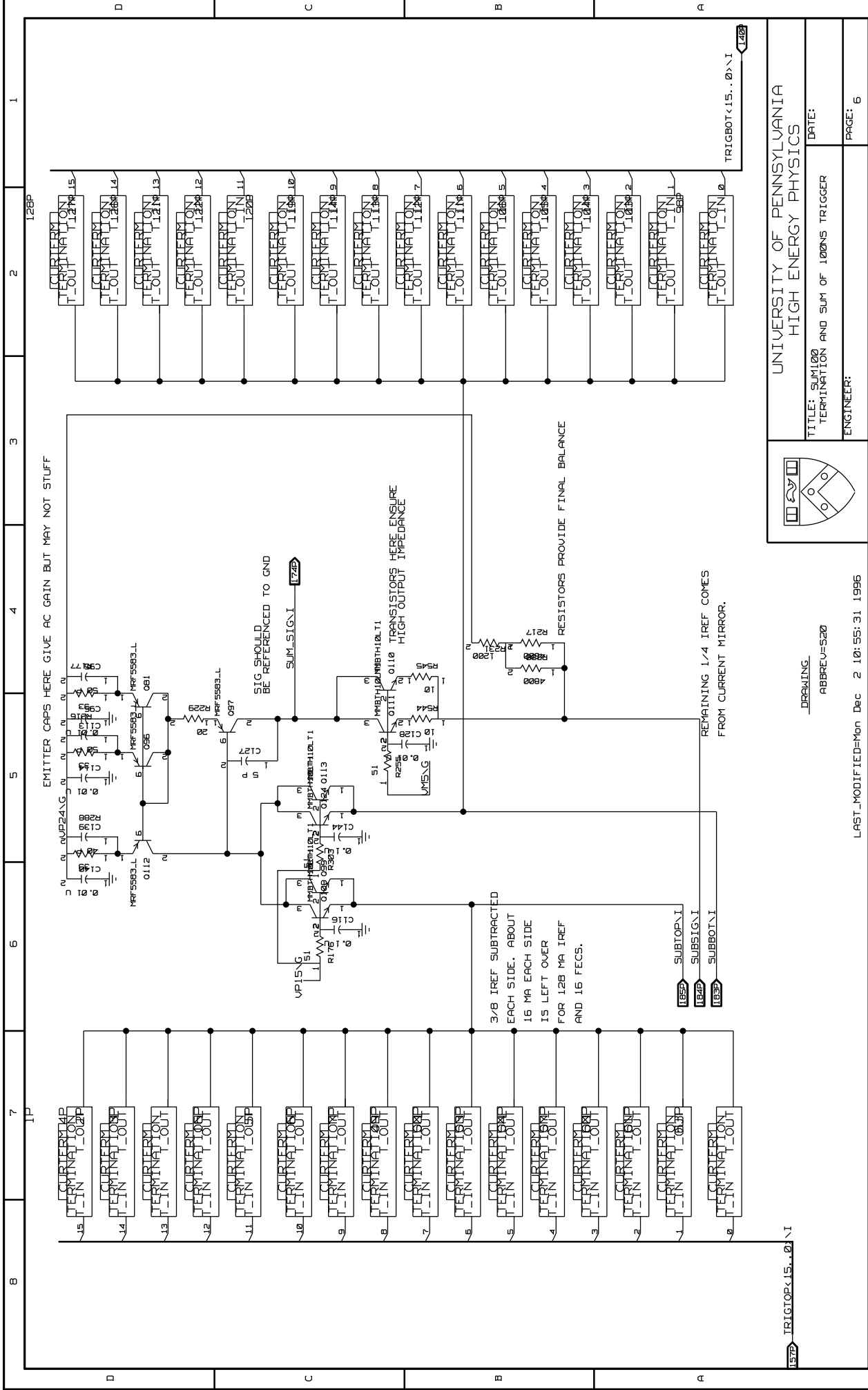UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS



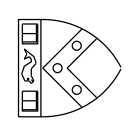UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS



TITLE: SUM100  
TERMINATION AND SUM OF 100NS TRIGGER



DATE:

ENGINEER:

PAGE: 6

DRAWING  
ABBREV=S20


LAST\_MODIFIED=Mon Dec 2 10:55:31 1996

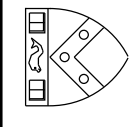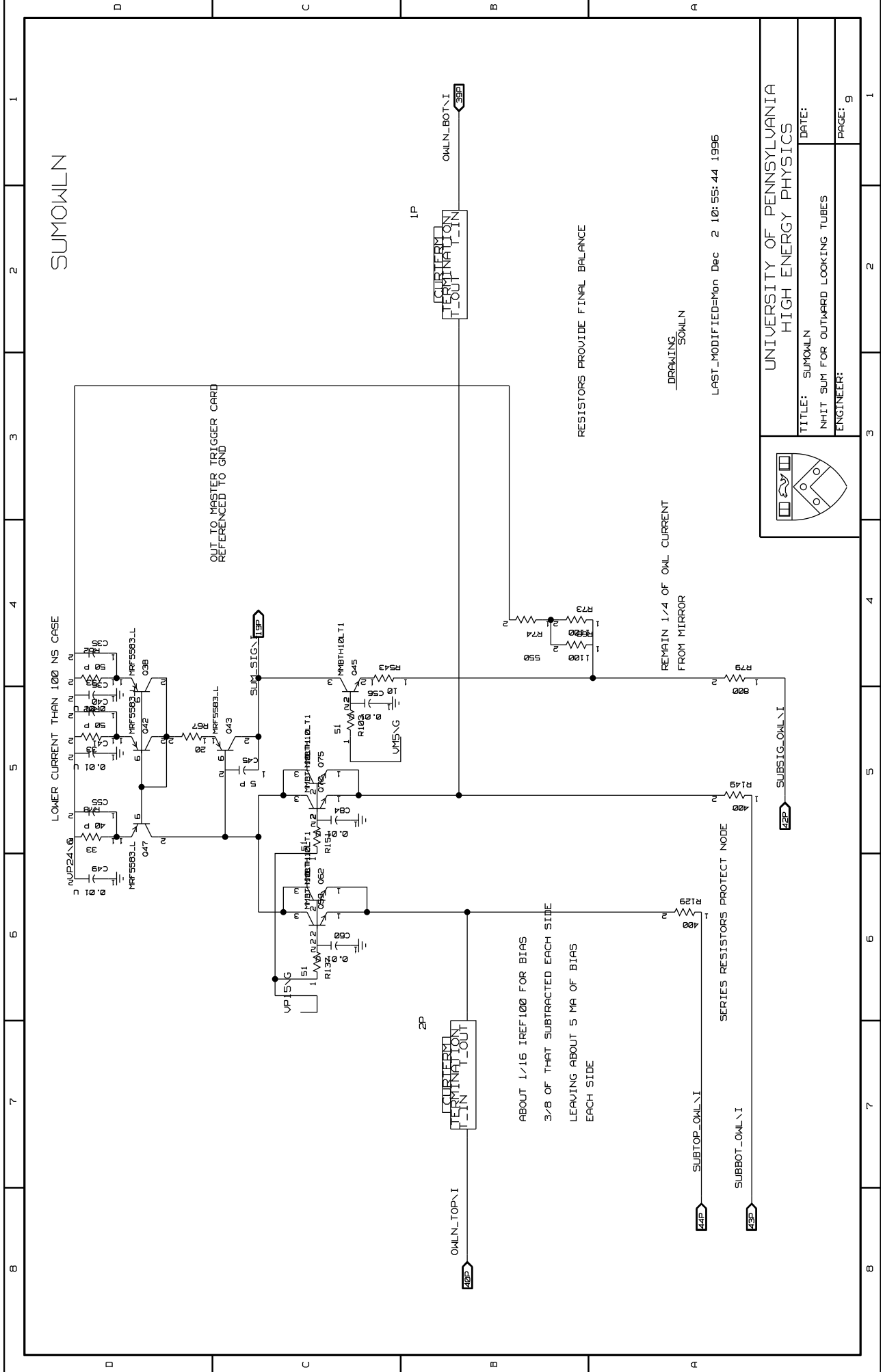


UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS

TITLE: SUMOVLN  
NHLT SUM FOR OUTWARD LOOKING TUBES  
ENGINEER:


DATE:  
PAGE: 9

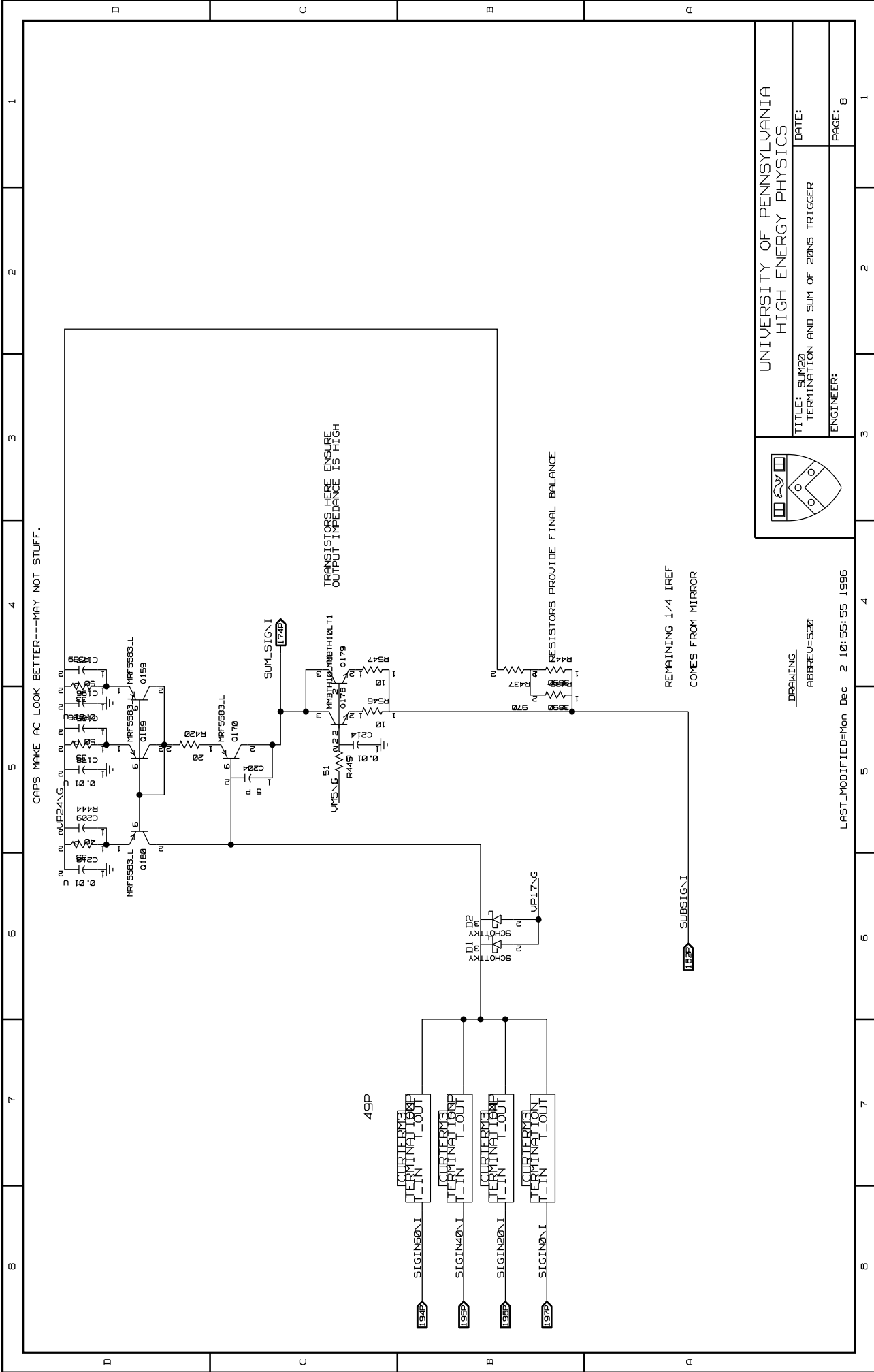

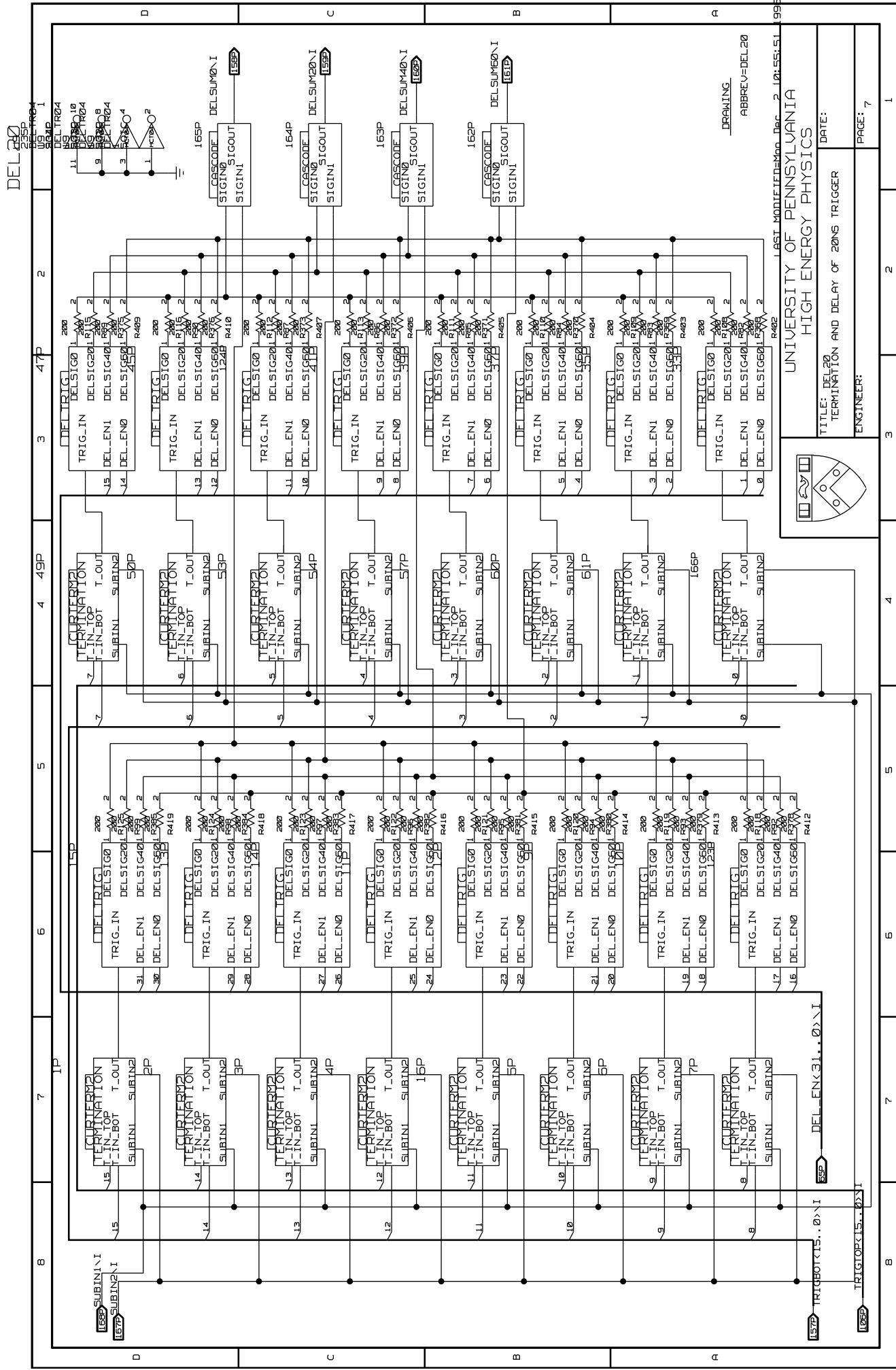




# SNOBUS

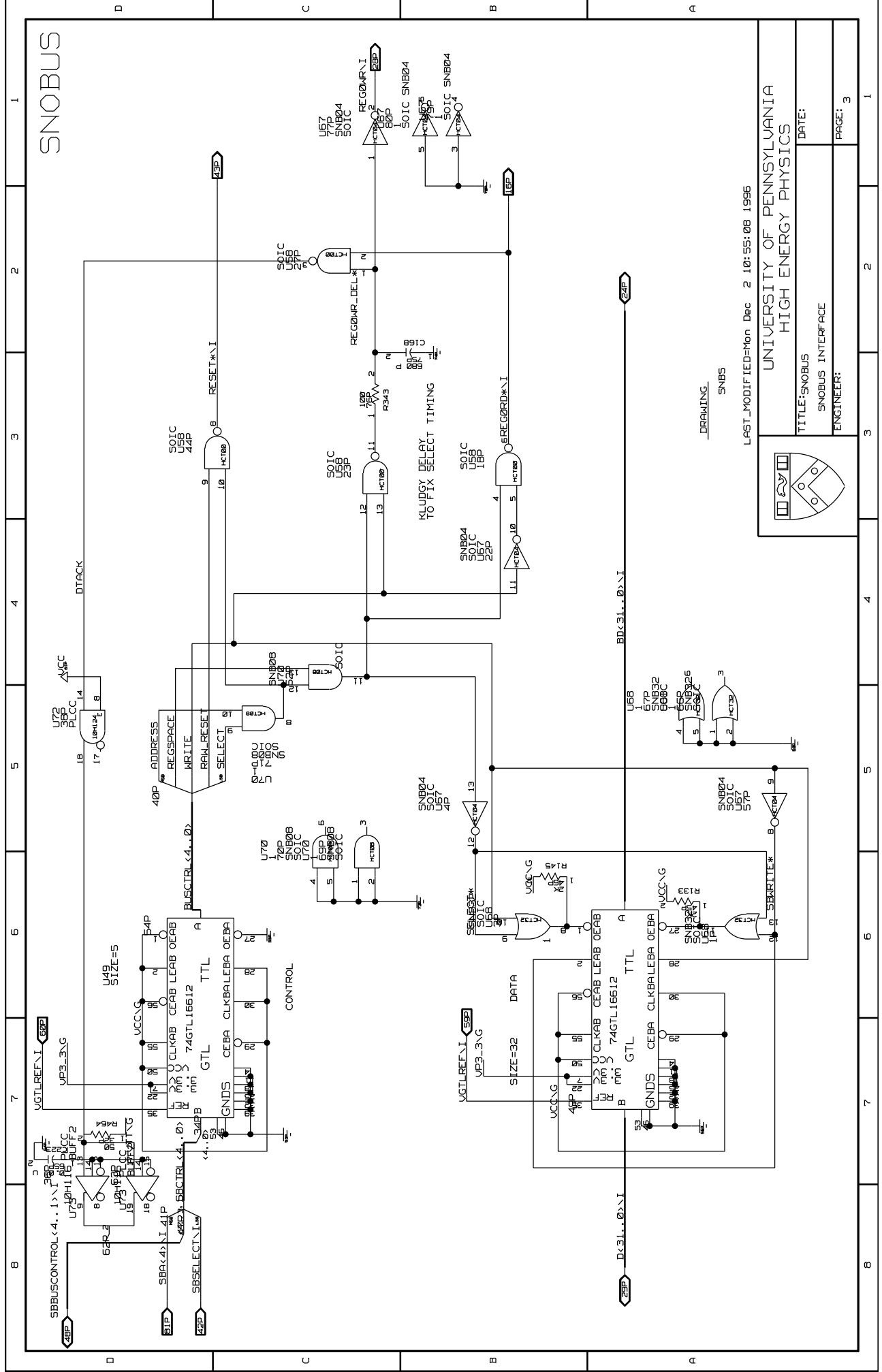

DRAWING:  
SNBS

LAST\_MODIFIED=Mon Dec 2 10:55:08 1996

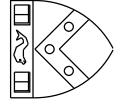


UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS

TITLE: SNOBUS  
SNOBUS INTERFACE  
ENGINEER:  
DATE:  
PAGE: 3







1	2	3	4	5	6	7	8
---	---	---	---	---	---	---	---

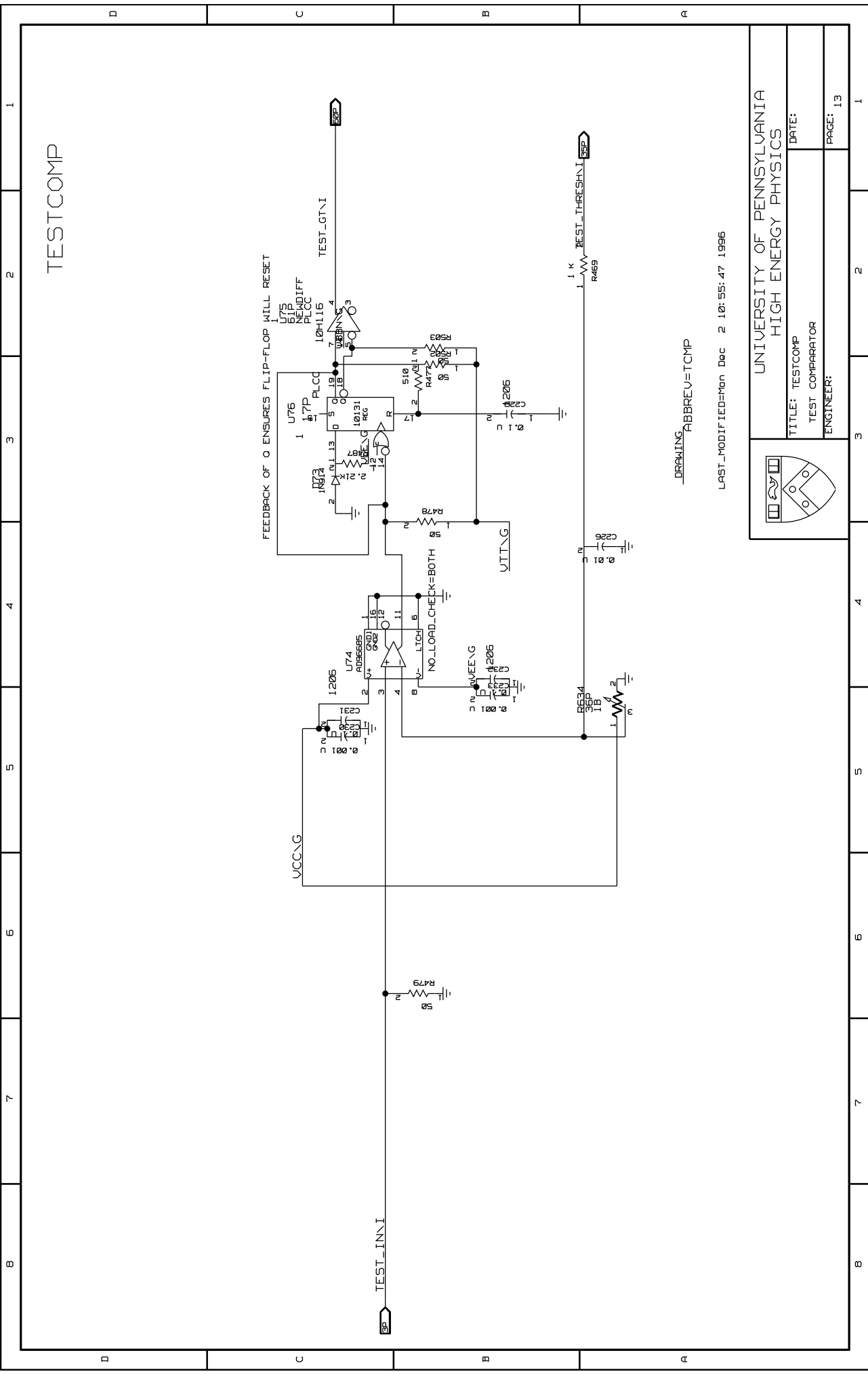

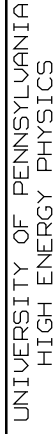
LAST_MODIFIED=Mon Dec 2 10:55:47 1996
---------------------------------------



PAGE: 13

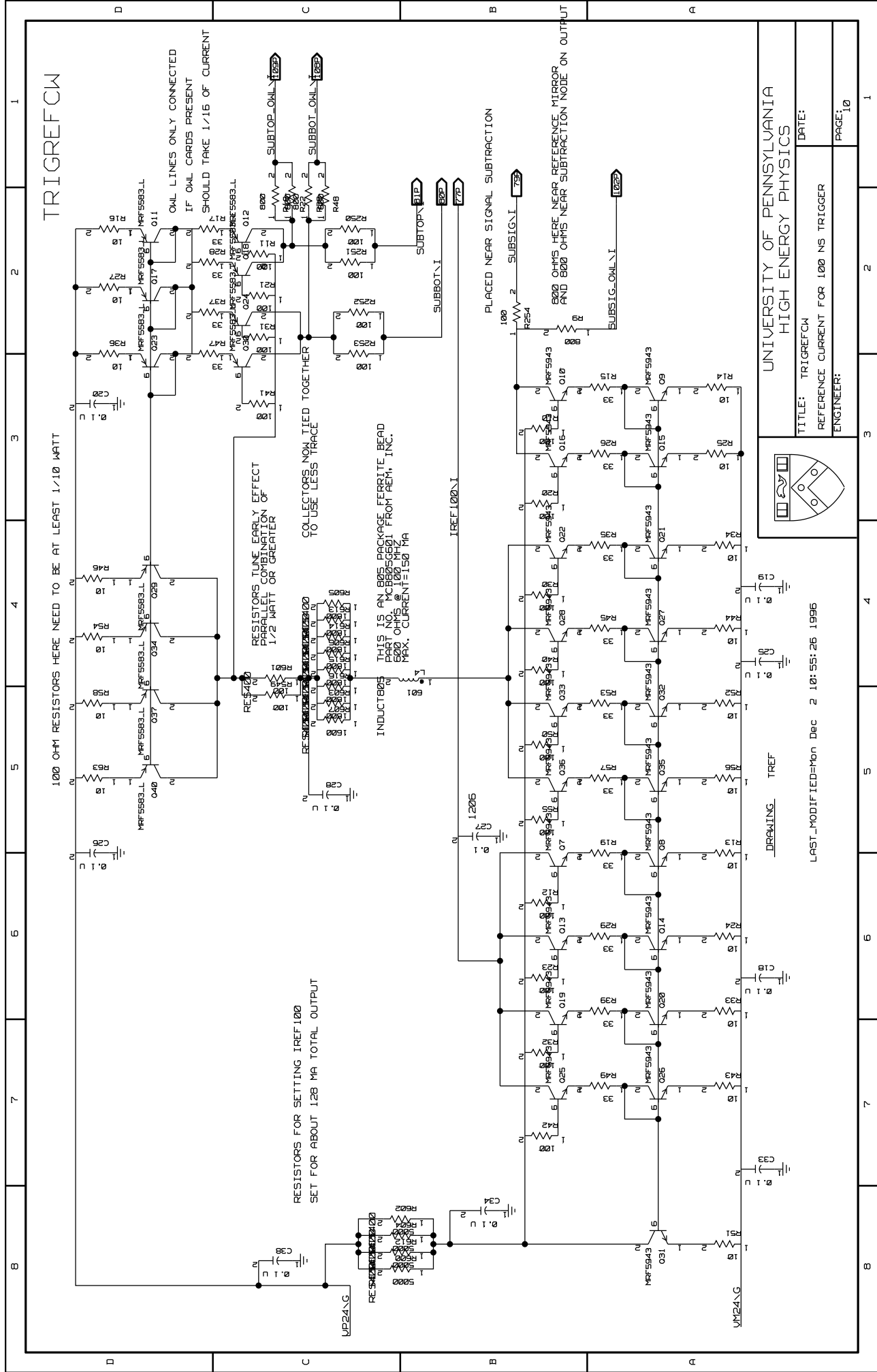

BP

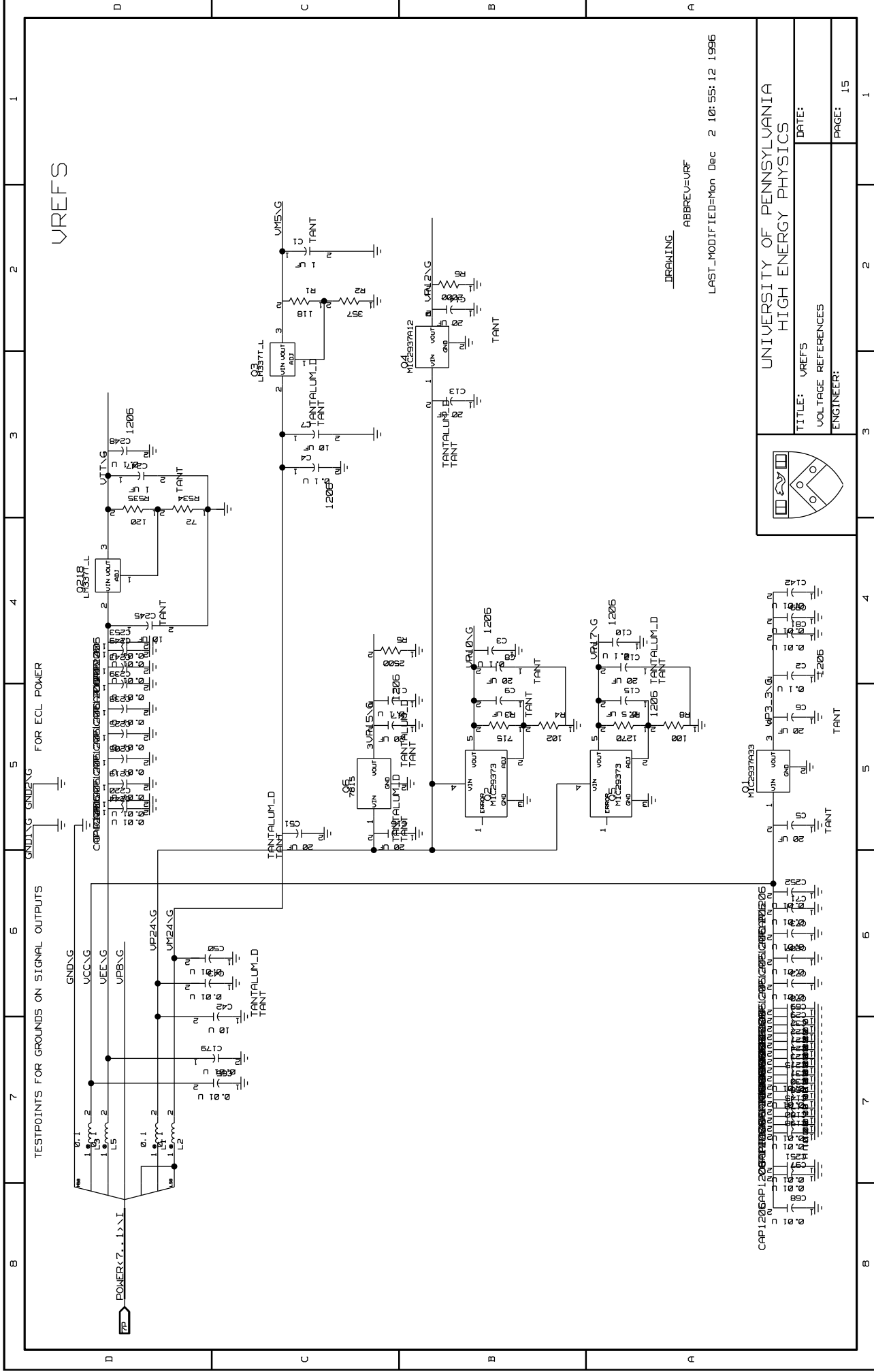




LAST\_MODIFIED=Mon Dec 2 10:55:12 1996

DRAWING  
ABBREV=VRF






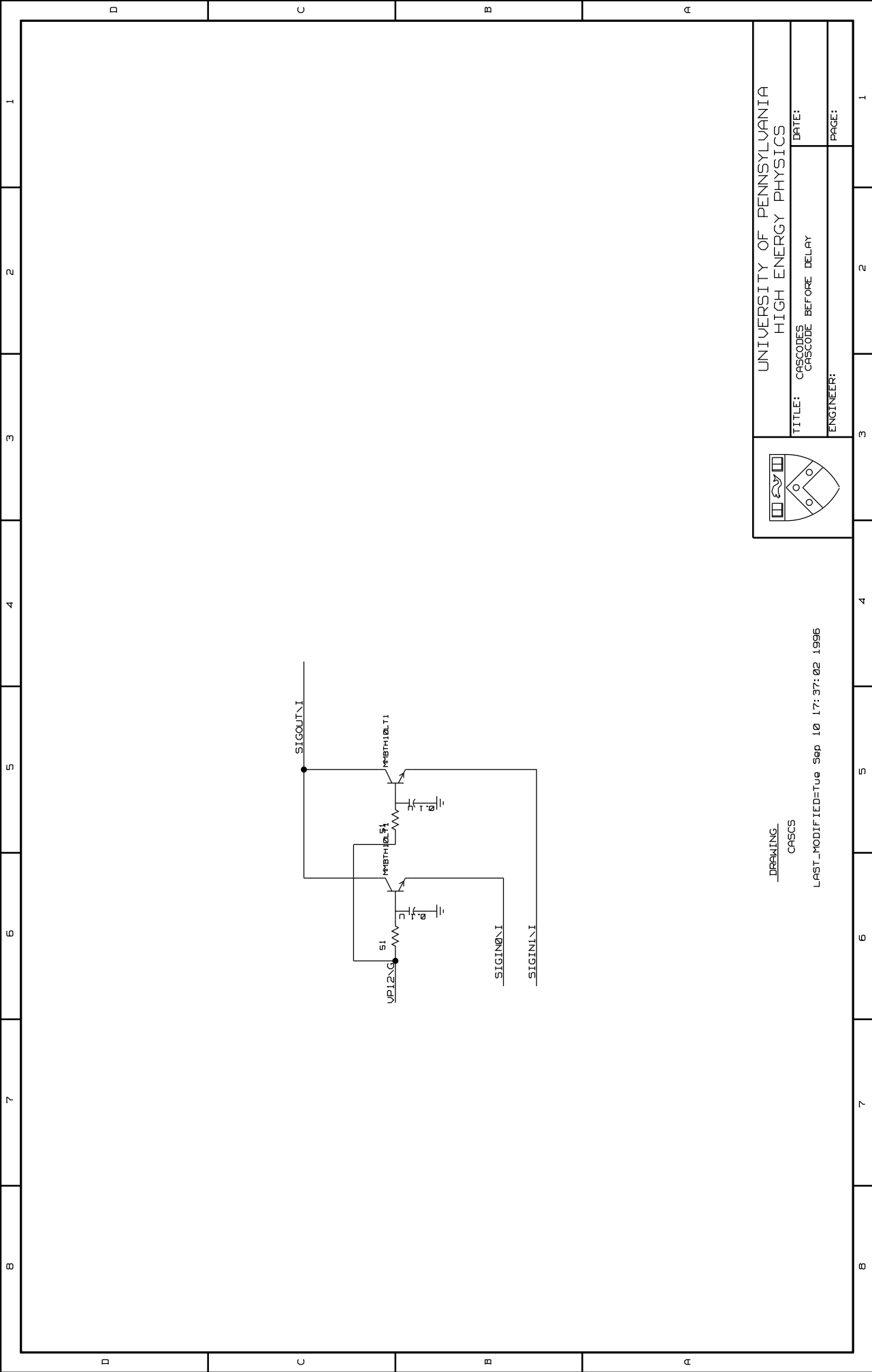

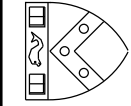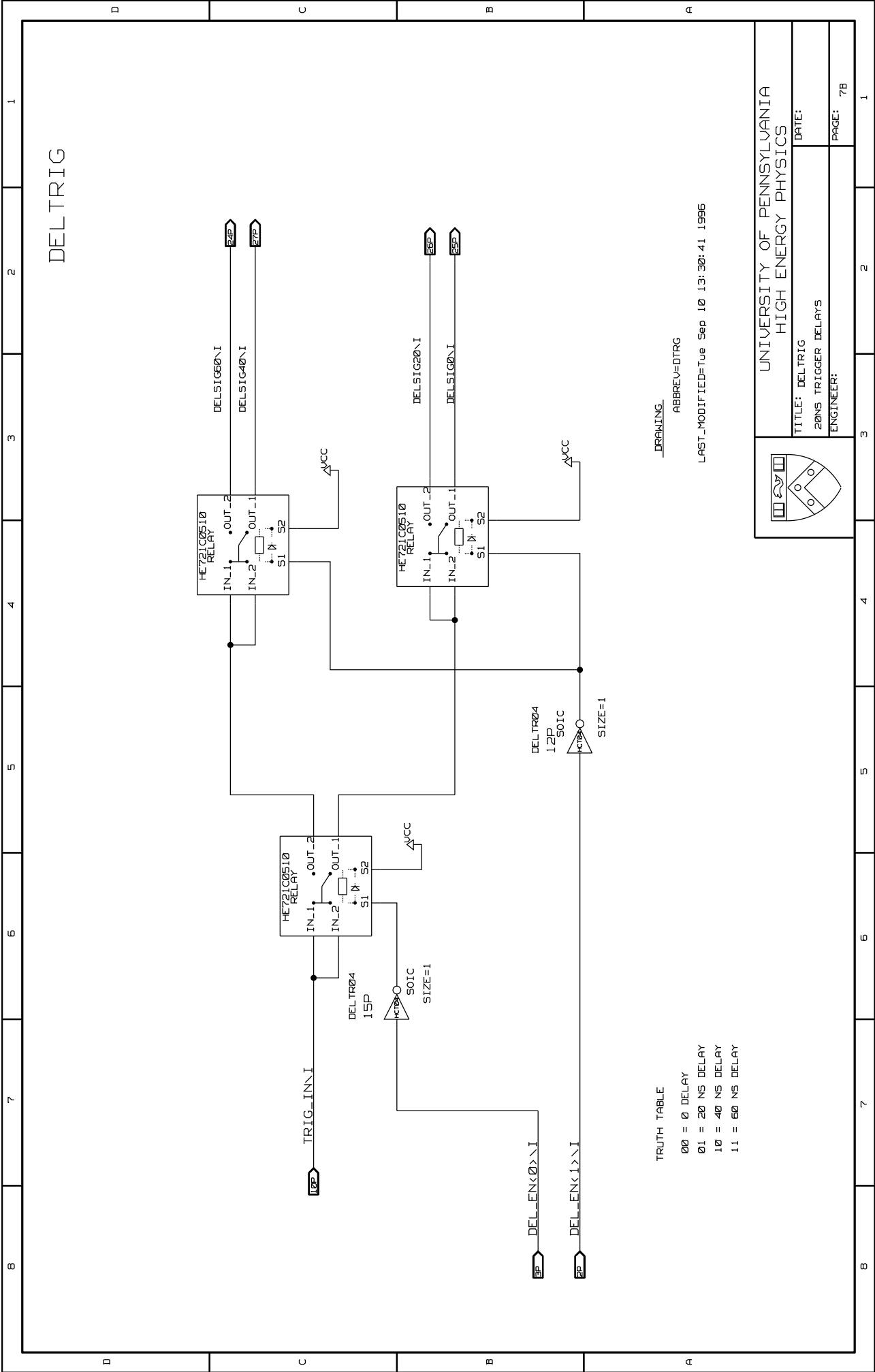


UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS

TITLE: DELTRIG	DATE:
20NS TRIGGER DELAYS	
ENGINEER:	PAGE: 7B

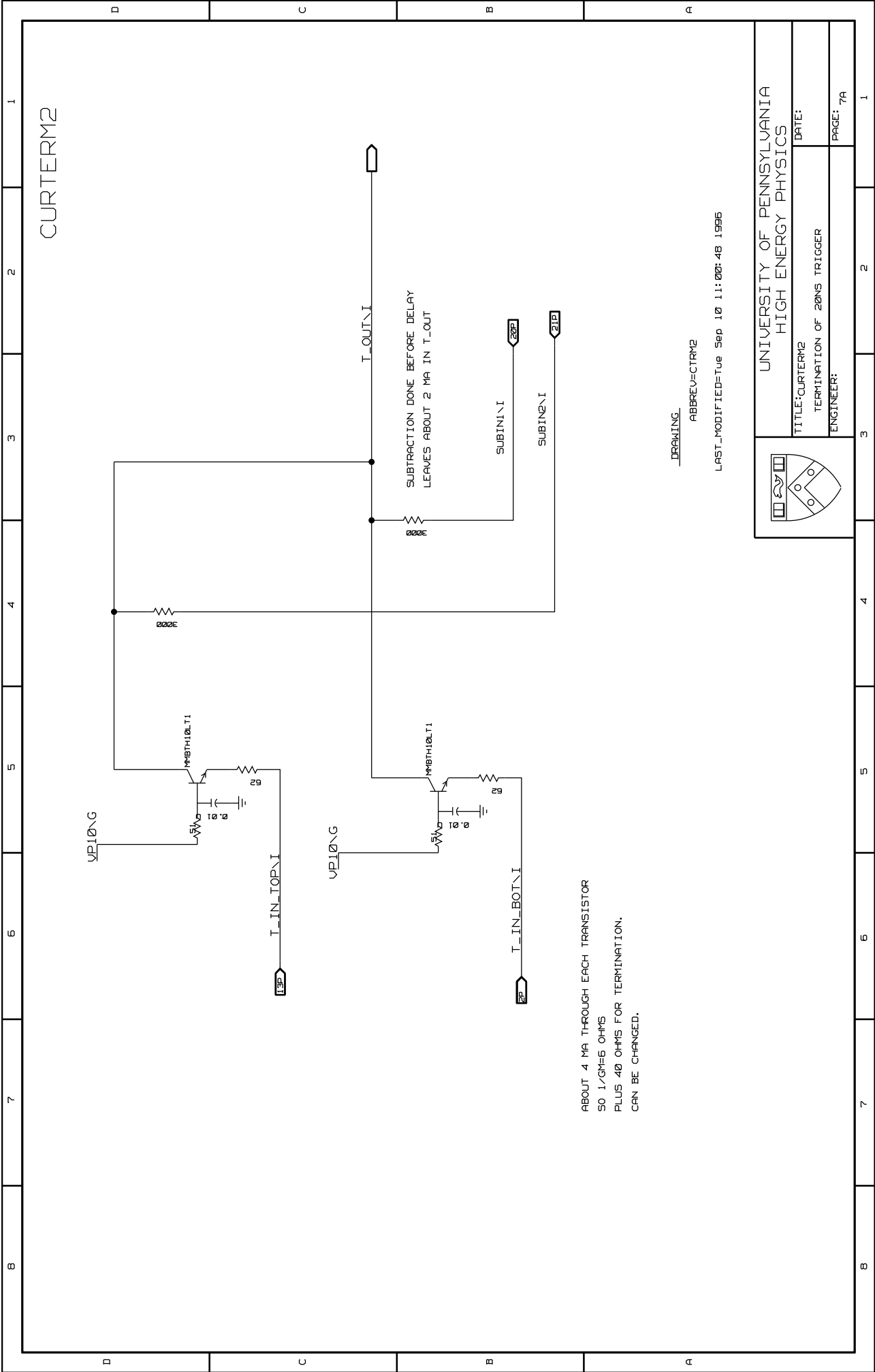



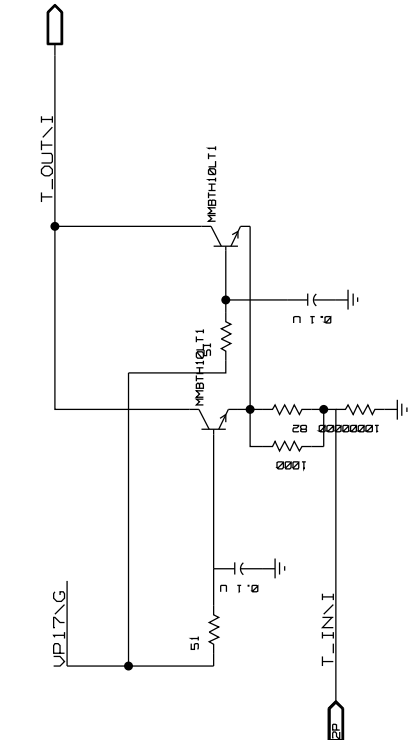


8	7	6	5	4	3	2	1
CURTERM3							
 <p>PARALLEL COMBINATION OF 1K AND 82 OHMS GIVES TUNABLE 75 OHM TERMINATION</p>							
<p><u>DRAWING</u> ABBREV=CTRM3 LAST_MODIFIED=Mon Sep 9 17:08:06 1996</p>							
<p>UNIVERSITY OF PENNSYLVANIA HIGH ENERGY PHYSICS</p> <p>TITLE: CURTERM3 TERMINATION OF 20NS TRIGGER ENGINEER: BA</p> <p>DATE: PAGE: BA</p>							
8	7	6	5	4	3	2	1





8	7	6	5	4	3	2	1
TABLE OF CONTENTS							
1...ROOT SHEET							
2							
2.1 MIDDLE BACKPLANE CONNECTOR							
2.2 J3 BACKPLANE CONNECTOR							
3...SNOBUS INTERFACE							
4...DELAY REGISTER							
5...CURRENT SUM FOR ENERGY TRIGGER							
6...CURRENT SUM FOR 100 NS TRIGGER							
6A TERMINATION FOR 100 NS TRIGGER SIGNAL							
7...TERMINATION AND DELAY FOR 20 NS TRIGGER SIGNAL							
7A TERMINATION AND SUM OF 20 NS TOP/BOTTOM TRIGGER SIGNAL							
7B 20 NS TRIGGER DELAY RELAYS							
7.B.1 20 NS DELAY							
7.B.2 40 NS DELAY							
8...TERMINATION AND SUM OF 20 NS TRIGGER SIGNAL							
8A TERMINATION OF 20 NS SIGNAL AFTER DELAY							
9 TERMINATION AND SUM OF OUTWARD LOOKING TUBE TRIGGER SIGNAL							
10...CURRENT REFERENCE FOR 100 NS AND OWL TRIGGER SIGNAL							
11...CURRENT REFERENCE FOR 20 NS TRIGGER SIGNAL							
12...TERMINATION BLOCK FOR BACKPLANE SIGNALS							
13...COMPARATOR FOR TRIGGER TESTS							
14...LEDS FOR TRIGGER MONITORING							
15...VOLTAGES							

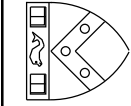

UNIVERSITY OF PENNSYLVANIA  
HIGH ENERGY PHYSICS

TITLE:

DATE:

ENGINEER:

PAGE: